

1. (30%) Consider the circuit shown in Fig. 1(a).

(a) (10%) Please find the current i flowing through the resistor $5\ \Omega$.

(b) (20%) Consider now that a load resistor is added to the circuit, as shown in Fig. 1(b).

We want to design the load resistance R_L such that it will receive maximum power.

Please give a procedure for finding R_L . **Note:** You do **not** need to find the value of

R_L . Only a procedure is required.

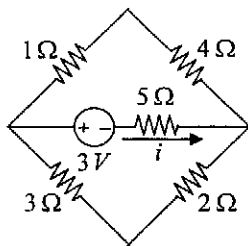


Fig. 1(a)



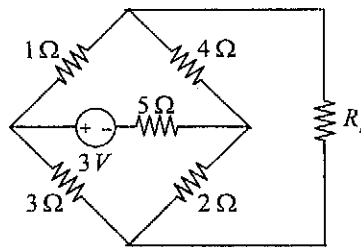


Fig. 1(b)

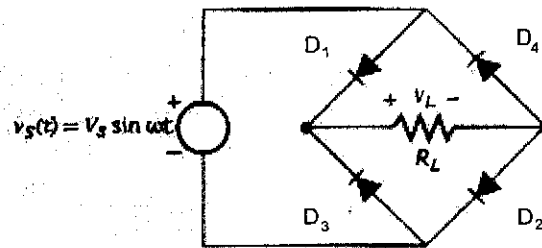2. (10%) Consider the following bridge rectifier. Describe its action as a full-wave rectifier, assuming the diodes to be ideal. In the figure, the input $v_s(t) = V_s \sin \omega t$.



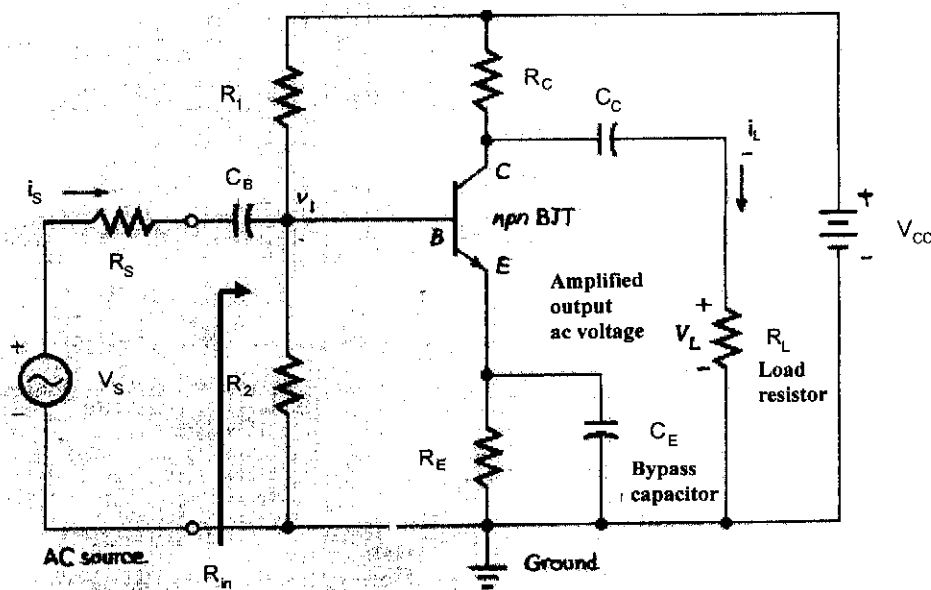3. (20%) Consider the following BJT circuit.



- (a) (5%) Describe the purpose of the capacitors C_B , C_C , and C_E .
- (b) (10%) Let $V_{CC} = 10 \text{ V}$, $R_1 = 18 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_C = 1 \text{ k}\Omega$, $R_E = 100 \Omega$. When $V_s = 0$.
Estimate the collector current (i.e., the current flowing into the collector) and V_{CE} of the BJT by assuming $i_B \approx 0$ and $V_{BE} \approx 0.5 \text{ V}$.
- (c) (5%) Draw the small-signal AC equivalent circuit of the BJT circuit.

4. (24%) Figure 4 shows an active circuit comprising Operational Amplifiers.

(a) (8%) Prove that this circuit, with input voltage e and output voltage u , functions as a phase-lead or phase-lag compensator.

(b) (8%) Choose parameters: R_1 , R_2 , R_3 , R_4 , C_1 and C_2 , so that the

transfer function of this circuit becomes $C(s) \equiv \frac{U(s)}{E(s)} = \frac{s+100}{s+10}$.

(c) (8%) Sketch the frequency response of the compensator $C(s)$ in (b) by means of Bode plot.

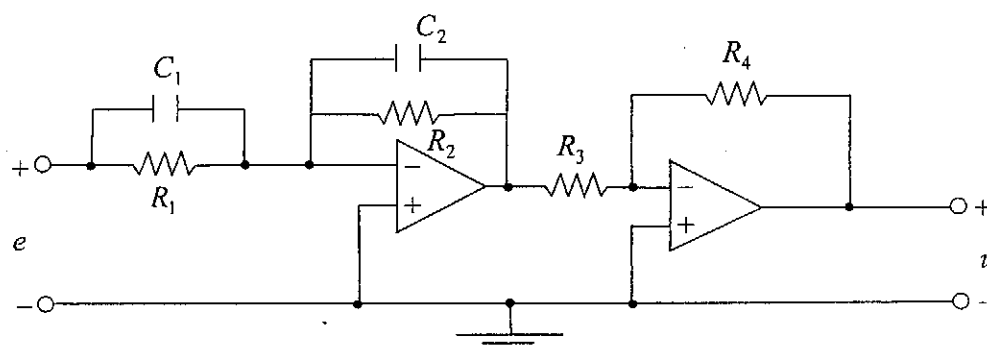


Figure 4. Lead or lag compensator

5. (16%) Answer the following fundamental questions about op-amp circuits:

(a) (8%) In active filters or analog computers, why is any operational amplifier always of *negative feedback* (i.e. the output is connected back to the Inverting input), instead of positive feedback or no feedback?

(b) (8%) Under what conditions are active compensators in place of passive filters to do signal processing?