

1. (40%) Consider the circuit shown in Fig. 1(a) and Fig. 1(b).
 - (a) (20%) For Fig. 1(a), please find the current i flowing through the resistor 3Ω using the method of mesh current analysis.
 - (b) (20%) Consider now the circuit of Fig. 1(b). Can we find the current i using the method of mesh current analysis? If yes, please define the required mesh currents. If no, please suggest a feasible method and provide a procedure for solving the problem.
Note: You do **not** need to find the value of i . Only a procedure is required.

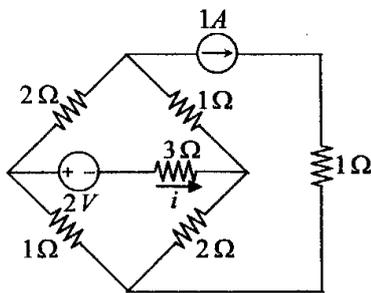


Fig. 1(a)

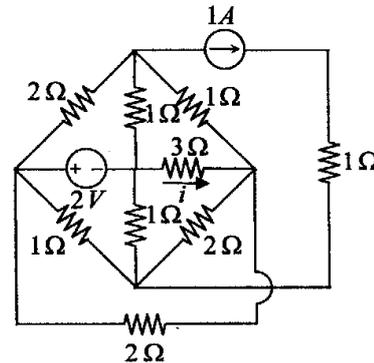


Fig. 1(b)

2. (15%) Consider the circuit shown in Fig. 2.
 - (a) (10%) Find an expression for the voltage frequency response function

$$H_v(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$$

- (b) (5%) Please determine the undamped natural frequency and damping ratio of the above function $H_v(j\omega)$.

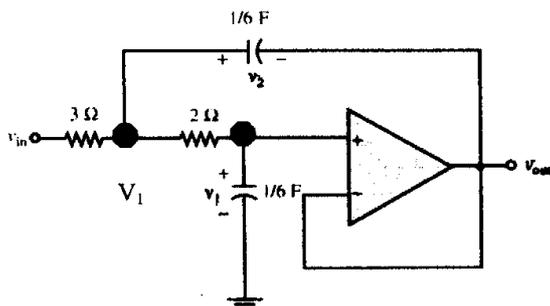


Fig. 2

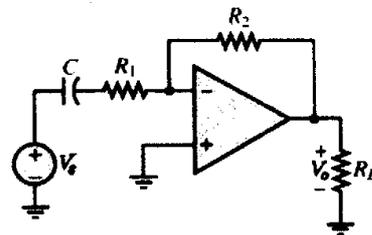


Fig. 3

3. (15%) For the circuit shown in Fig. 3, where $C=1\mu\text{F}$, $R_1=1.8\text{K}\Omega$, $R_2=8.2\text{K}\Omega$, $R_L=333\Omega$. Please answer the following questions.
 - (a) (5%) Is the circuit is a low- or high-pass filter?
 - (b) (5%) Please find the gain V_o/V_s in decibel in the passband.
 - (c) (5%) Please find the cutoff frequency.

4. (10%) Consider the circuit shown in Fig. 4. Assume that both transistors are silicon-based with $\beta = 100$. Please determine V_{CE1} and V_{CE2} (the voltage from collector to emitter of the transistors Q_1 and Q_2 , respectively).

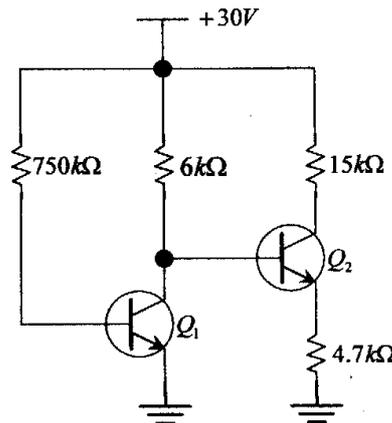


Fig. 4

5. (20%) Consider the circuit shown in Fig. 5, where $V_{DD} = 30\text{ V}$, $R_D = 10\text{ k}\Omega$, $R_1 = R_2 = 1\text{ M}\Omega$. Assume that the transistor possesses a threshold voltage of $V_T = 4\text{ V}$ and conductance parameter of $K = 0.2188\text{ mA/V}^2$. Determine the appropriate value of R_S such that the operating point $V_{DS} = 8\text{ V}$.

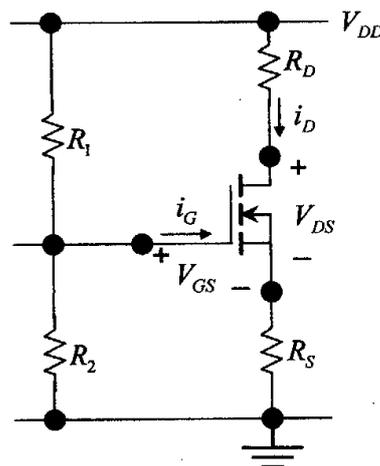


Fig. 5