

1. (30%) Consider a rectifier circuit shown in Fig. 1, where the diode is assumed to be ideal.

(a) (10%) Please plot the waveform of the output voltage $V_o(t)$.

(b) (15%) Consider now a capacitor is added to the circuit, as shown in Fig. 2. Two cases of capacitor are considered:

(i) $C = 1\mu\text{F}$; (ii) $C = 0.01\text{F}$

Which capacitor can make the output voltage closer to DC output (i.e., the output waveform more flat)? State the reasons. No score will be given without reasons.

(c) (5%) Suppose now that the diode is not ideal. Please discuss the effects of actual diode.

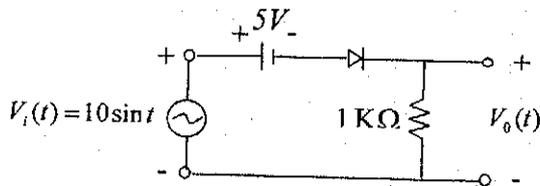


Fig. 1

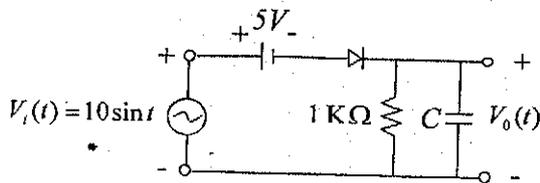


Fig. 2

2. (10%) The instrumentation amplifier has widespread applications. Please determine the voltage gain $A_v = \frac{v_o}{v_1 - v_2}$ of the instrumentation amplifier circuit shown in Fig. 3.

(Assume ideal op-amps)

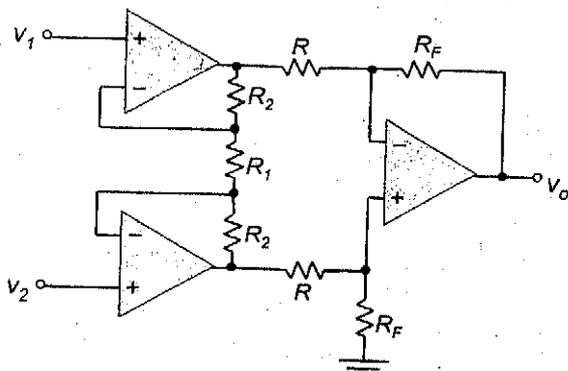


Fig. 3

3. (20%) In many op-amp applications, one is to use as a voltage-to-current converter. Fig. 4 shows a voltage-to-current converter circuit. Please answer the following questions (*the ideal op-amp is assumed*)
- (10%) Please derive the relation $a \cdot i_L = b \cdot v_i$, where a is the function of R_1, R_2, R_3, R_F, Z_L ; b is the function of R_1, R_3, R_F ; v_i is the input voltage; i_L is the current flowing through Z_L (see Fig. 2).
 - (5%) According to the result derived in question 2(a), at what kind of condition, we can design the circuit such that i_L is independent of Z_L ? (*Hint: think about how to adjust the coefficient of Z_L*)
 - (5%) Let $Z_L = 100\Omega$, $R_1 = 10k\Omega$, $R_2 = 1k\Omega$, $R_3 = 1k\Omega$, and $R_F = 10k\Omega$. If $v_i = -5V$, determine the output voltage v_o .

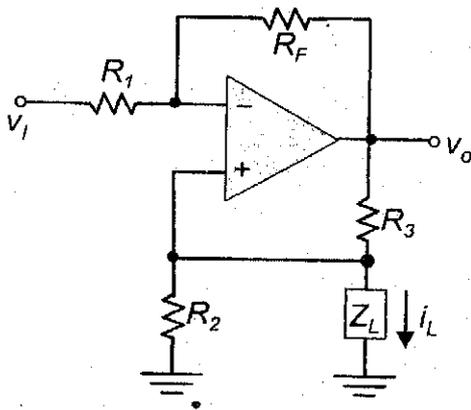


Fig. 4

4. (10%) The BJT circuit is shown in Fig. 5. Let the $V_{BE} = 0.6V$ and the current amplification factor $\beta = 100$. Please find the V_{CE} and determine the operating mode of the BJT.

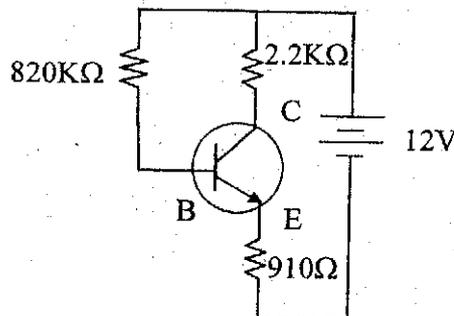


Fig. 5

- (5) (30%) Determine the operating Q point in the n-channel enhancement mode MOSFET circuit given as Fig. 6 below. The circuit parameters are given as $V_{DD}=36V$; $R_D=10\Omega$, $R_1=R_2=2M\Omega$, $V_T=4V$; $K=0.1mA/V^2$. Here K is the conductance parameter. The operating condition is to assume that $V_{DSQ}=V_{DD}/2=18V$.
- (a) (10%) Determine V_{GG} , R_s , and i_{DQ} .
- (b) (10%) What is the operating region of the MOSFET?
- (c) (10%) Draw the circuit of the common-source amplifier using the N -MOS. Draw the small-signal equivalent circuit of the amplifier. Explain the parameter in the equivalent circuit.

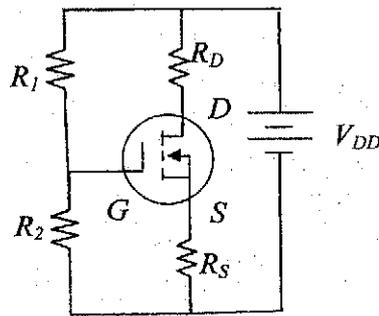


Fig. 6